

1. Instrumentation Amplifier

A three Op-Amps instrumentation Amplifier is shown in Figure 1. Three Op-Amps instrumentation amplifiers are popular because they offer high input resistance, adjustable differential gain, and high common mode rejection ratio (CMRR).

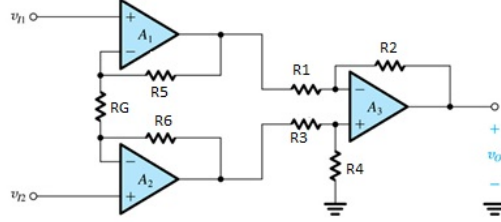


Figure 1: An Instrumentation Amplifier

To decrease the number of unknowns, R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 are usually made equal R . The differential gain of the amplifier ($A_d = \frac{v_o}{v_{I2} - v_{I1}}$) can be determined by Eq.1.

$$A_d = 1 + \frac{2R}{R_G} \quad (1)$$

The common mode gain of the instrumentation amplifier can be determined by driving both v_{I2} and v_{I1} with the same source (e.g. v_{icm}) and calculating v_o/v_{icm} .

$$A_c = \frac{v_o}{v_{icm}} = \frac{R_4}{R_3 + R_4} \frac{R_1 + R_2}{R_1} - \frac{R_2}{R_1} \quad (2)$$

A_c is zero in theory since $R_i = R$ for $i = 1, 2 \dots 6$. But in practice, A_c is not zero because the resistors can not be perfectly matched.

The common rejection ratio (CMRR) in decibels can be calculated by

$$CMRR = 20 \log_{10} \frac{A_d}{|A_c|} \quad (3)$$

The probability that a resistor is within 1 percent of its nominal value is

$$P[0.99R_n < R_n \leq 1.01R_n] = \Theta\left(\frac{0.01R_n}{\sigma_{R_n}}\right) - \Theta\left(\frac{-0.01R_n}{\sigma_{R_n}}\right) = 2\Theta\left(\frac{0.01R_n}{\sigma_{R_n}}\right) - 1 \quad (4)$$

R_n is the nominal value of a resistor. $\frac{0.01R_n}{\sigma_{R_n}}$ is the standard normal random variable (i.e. z).

Submission checklist:

- (a) (Extra credit, 1 point) Derive Eq. 1.
- (b) (Extra credit, 1 point) Derive Eq. 2.
- (c) (1 points) Let $R = 10 \text{ K}\Omega$. What should be the value of R_G in order to obtain 60 dB of differential gain?
- (d) (2 points) Model R_i , $i = 1, 2 \dots 6$ as a Gaussian random variable with a mean of μ_{R_i} and a standard deviation of σ_{R_i} . How is μ_{R_i} related to σ_{R_i} if the probability that R_i is within one percent of μ_{R_i} is 0.99?
- (e) (3 points) Generate a histogram of CMRR of one million instrumentation amplifiers in matlab. Please submit the plot along with the code.

2. Common Rejection Ratio of a Differential Pair

The small signal equivalent circuit of a differential pair is shown in Figure 2. R_{SS} represents the resistance of the current source. If all of the transistors and resistors are perfectly matched, then the common rejection ratio of a differential pair is ∞ . Otherwise, the common rejection ratio is finite. We will explore the mismatch due to the transconductance of the transistor in this problem. Let g_{m1} and g_{m2} be the transconductance of Q_1 and Q_2 respectively.

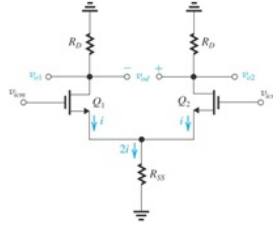


Figure 2: A Differential Amplifier

The output voltage of v_{o1} is

$$v_{o1} = -\frac{g_{m1}R_D}{1 + (g_{m1} + g_{m2})R_{SS}}v_{icm} \quad (5)$$

The output voltage of v_{o2} is

$$v_{o2} = -\frac{g_{m2}R_D}{1 + (g_{m1} + g_{m2})R_{SS}}v_{icm} \quad (6)$$

The differential output voltage v_{od} is then

$$v_{od} = \frac{(g_{m1} - g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}}v_{icm} \quad (7)$$

The common-mode gain of the differential amplifier is

$$A_c = \frac{(g_{m1} - g_{m2})R_D}{1 + (g_{m1} + g_{m2})R_{SS}} \quad (8)$$

It can be shown that the differential gain of the diff pair is

$$A_d = g_m R_D \quad (9)$$

The common mode rejection ratio (CMRR) is

$$CMRR = \frac{A_d}{A_c} \quad (10)$$

CMRR can be expressed in dB by $20 \log_{10}(CMRR)$.

Assume that $R_D=5 \text{ K}\Omega$ and $R_{SS}=25 \text{ K}\Omega$. Assume that g_{m1} and g_{m2} can be modeled as Gaussian random variable. Let g_m (i.e. μ_{g_m} be 1 mA/V with a standard deviation of 0.1 mA/V. Generate a hisotram of one million differential pairs. What is the average CMRR in dB? (5 points)